

Quiz 2

Electrical Circuits 1


TE1002

Tecnológico de Monterrey

Dr. Juan-Manuel CAMPOS-SANDOVAL

Name _____

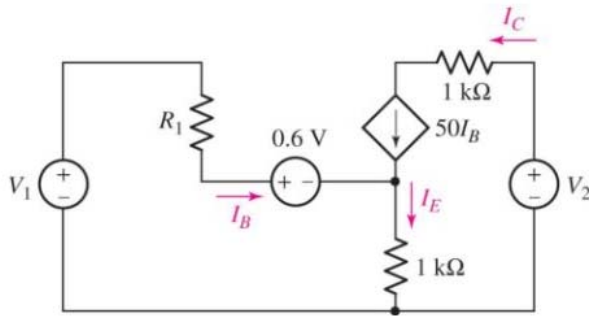In the given circuit, calculate the voltage across the dependent source ("+" reference on top) if V_2 is 15 V, and I_B is 20 μA .



The voltage across the dependent source is