

Quiz 5 (mesh and supermesh)

Electrical Circuits 1


TE1002

Tecnológico de Monterrey

Dr. Juan-Manuel CAMPOS-SANDOVAL

Name _____

Consider the circuit given below.

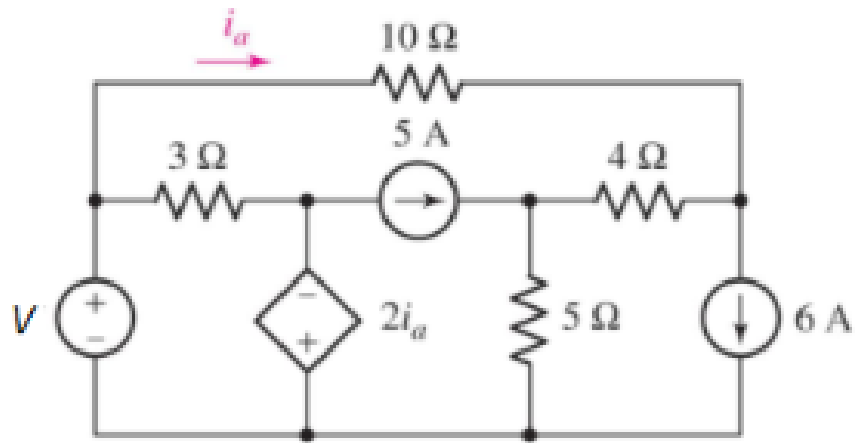

If $V = 4$ V, determine the power absorbed by the 10-Ω resistor.