

Quiz 5 Solution (mesh and supermesh)

Electrical Circuits 1


TE1002

Tecnológico de Monterrey

Dr. Juan-Manuel CAMPOS-SANDOVAL

Name _____

Consider the circuit given below.

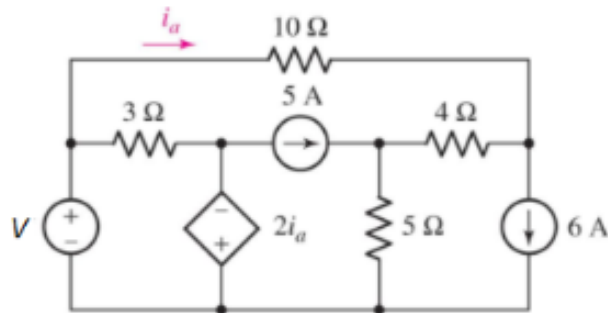

If $V = 4$ V, determine the power absorbed by the 10- Ω resistor.

The value of the power absorbed by the 10- Ω resistor is W.

Explanation:

With the top node naturally associated with a clockwise mesh current i_a , we name (left to right) the remaining mesh currents (all defined flowing clockwise) as i_1 , i_2 and i_3 , respectively.

We create a supermesh from meshes "a" and "2", noting that $i_3 = 6$ A based on inspection.

The mesh equations are

$$-4 + 3i_1 - 2i_a - 3i_a = 0$$

$$2i_a + 3i_a - 3i_1 + 10i_a + 4i_a - (4 \times 6) + 5i_2 - (5 \times 6) = 0$$

$$i_2 - i_a = 5$$

On solving the simultaneous equations, we get

$$i_a = 1.7368 \text{ A}$$

$$i_1 = 4.2281 \text{ A}$$

$$i_2 = 6.7368 \text{ A}$$

$$P_{10\Omega} = 10 \times i_a^2 = 30.1662 \text{ W}$$

The value of the power absorbed by the 10- Ω resistor is 30.1662 W.