

Quiz 6 (Thévenin & Norton)

Electrical Circuits 1

TE1002

Tecnológico de Monterrey

Dr. Juan-Manuel CAMPOS-SANDOVAL

Name _____

Determine the Thévenin and Norton equivalents of the given circuit, as seen by an unspecified element connected between terminals a and b . In the given circuit, $V_x = 0.2v_{ab}$.

