

Quiz 7 Solution (Δ -Y conversion)

Electrical Circuits 1



TE1002

Tecnológico de Monterrey

Dr. Juan-Manuel CAMPOS-SANDOVAL

Name _____

Δ -Y (delta-wye) Conversion₂

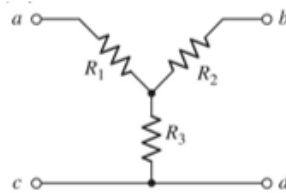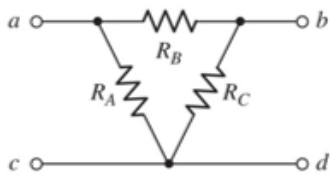

This Δ is equivalent to the Y if

This Y is equivalent to the Δ if

$$\begin{aligned} R_A &= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} \\ R_B &= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} \\ R_C &= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} \end{aligned}$$

$$\begin{aligned} R_1 &= \frac{R_A R_B}{R_A + R_B + R_C} \\ R_2 &= \frac{R_B R_C}{R_A + R_B + R_C} \\ R_3 &= \frac{R_C R_A}{R_A + R_B + R_C} \end{aligned}$$

Solve using Y to delta conversión

Copyright © McGraw-Hill Education. Permission required for reproduction or display.

