

Solution Second Partial Integrator Exam

TE1002 Circuits 1


Dr. Juan Manuel CAMPOS

Tecnológico de Monterrey

Name _____

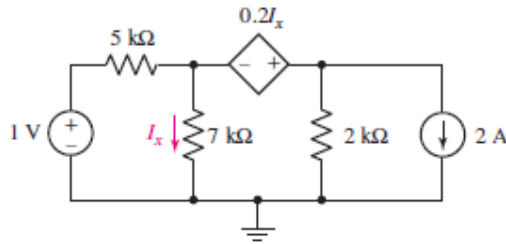Problem 1 (15 points)

Employ superposition principles to obtain a value for the current I_x as labeled in Fig. 5.56.



■ FIGURE 5.56

Solution Problem 1

We select the bottom node as the reference, then identify v_1 with the lefthand terminal of the dependent source and v_2 with the righthand terminal.

Via superposition, we first consider the contribution of the 1 V source:

$$\frac{v_1' - 1}{5000} + \frac{v_1'}{7000} + \frac{v_2'}{2000} = 0 \quad \text{and}$$

$$\left(1 + \frac{0.2}{7000}\right)v_1' - v_2' = 0$$

Solving, $v_1' = 0.237$ V

Next, we consider the contribution of the 2 A source:

$$\frac{v_1''}{5000} + \frac{v_1''}{7000} + \frac{v_2''}{2000} = -2 \quad \text{and}$$


$$\left(1 + \frac{0.2}{7000}\right)v_1'' - v_2'' = 0$$

Solving, $v_1'' = -2373$ V. Adding our two components, $v_1 = -2372.763$ V.

Thus, $i_x = v_1/7000 = -338.9661$ mA

Problem 2 (15 points)

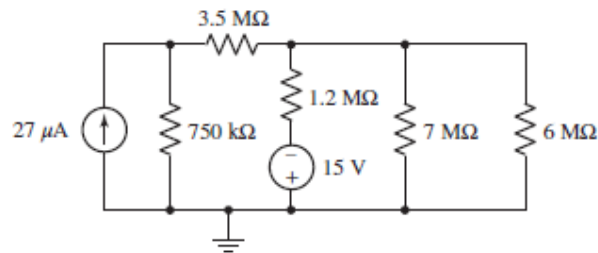(a) Using repeated source transformations, reduce the circuit of Fig. 5.62 to a voltage source in series with a resistor, both of which are in series with the $6\text{ M}\Omega$ resistor. (b) Calculate the power dissipated by the $6\text{ M}\Omega$ resistor using your simplified circuit.



■ FIGURE 5.62

Solution Problem 2

(a) Perform the following steps in order:


Combine the $27\text{ }\mu\text{A}$ and $750\text{ k}\Omega$ to obtain 20.25 V in series with $750\text{ k}\Omega$ in series with $3.5\text{ M}\Omega$.

Convert this series combination to a $4.25\text{ M}\Omega$ resistor in parallel with a $4.765\text{ }\mu\text{A}$ source, arrow up.

Convert the $15\text{ V} / 1.2\text{ M}\Omega$ series combination into a $12.5\text{ }\mu\text{A}$ source (arrow down) in parallel with $1.2\text{ M}\Omega$. This appears in parallel with the current source from above as well as the $7\text{ M}\Omega$ and $6\text{ M}\Omega$.

Combine: $4.25\text{ M}\Omega \parallel 1.2\text{ M}\Omega \parallel 7\text{ M}\Omega = 0.8254\text{ M}\Omega$. This, along with the $-12.5\text{ }\mu\text{A} + 4.765\text{ }\mu\text{A}$ yield a $-7.735\text{ }\mu\text{A}$ source (arrow up) in parallel with $825.4\text{ k}\Omega$ in parallel with $6\text{ M}\Omega$.

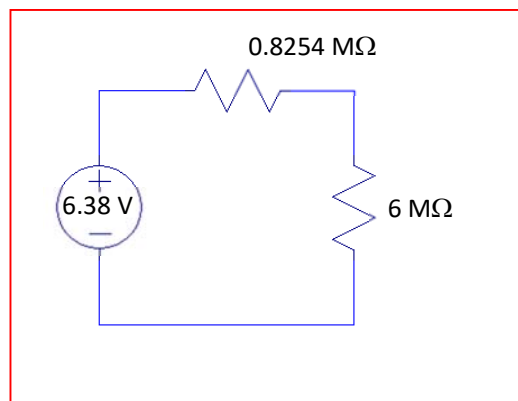Convert the current source and $825.4\text{ k}\Omega$ resistor into a 6.38 V source ('+' reference up) in series with $825.4\text{ k}\Omega$ and $6\text{ M}\Omega$.



(b) $P_{6\text{M}\Omega} = \left[\frac{6.38}{6 \times 10^6 + 825.4 \times 10^3} \right]^2 (6 \times 10^6) = 5.24\text{ }\mu\text{W}$

Problem 3 (20 points)

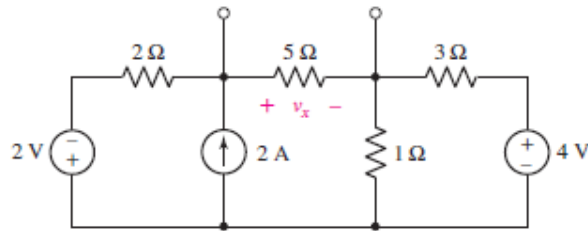


FIGURE 5.74

(a) Determine the Norton equivalent of the circuit depicted in Fig. 5.74 as seen looking into the two open terminals. (b) Compute power dissipated in a $5\ \Omega$ resistor connected in parallel with the existing $5\ \Omega$ resistor. (c) Compute the current flowing through a short circuit connecting the two terminals.

Solution Problem 3

(a) Employ nodal analysis:

$$2 = \frac{v_1 + 2}{2} + \frac{v_1 - v_2}{5} \quad [1]$$

$$0 = \frac{v_2 - v_1}{5} + v_2 + \frac{v_2 - 4}{3} \quad [2]$$

Solving, $v_1 = 54/31\ \text{V}$ and $v_2 = 34/31\ \text{V}$. Thus, $V_{\text{TH}} = v_X = v_1 - v_2 = 645.2\ \text{mV}$

By inspection, $R_{\text{TH}} = 5 \parallel [2 + 1 \parallel 3] = 1.774\ \Omega$

Thus, $i_N = v_{\text{TH}}/R_{\text{TH}} = 363.7\ \text{mA}$ and $R_N = R_{\text{TH}} = 1.774\ \Omega$


(b) $i_{\text{load}} = (0.3637)(1.774)/(5 + 1.774) = 95.25\ \text{mA}$

$$P_{\text{load}} = 5(i_{\text{load}})^2 = 45.36\ \text{mW}$$

(c) $363.7\ \text{mA}$

Problem 4 (20 points)

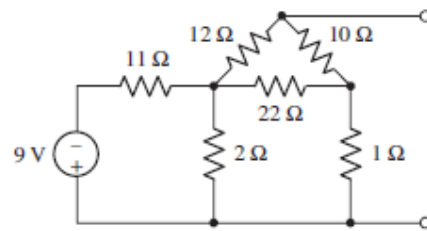(a) Determine the two-component Thévenin equivalent of the network in Fig. 5.102. (b) Calculate the power dissipated by a $1\ \Omega$ resistor connected between the open terminals.



■ FIGURE 5.102

Solution Problem 4

(a) Shorting the 9 V source leaves the $11\ \Omega$ in parallel with $2\ \Omega$.

Name this $R_A = 1.69\ \Omega$.

Then, $R_B = 22\ \Omega$, and $R_C = 1\ \Omega$.

Converting this to a T network, with $R = R_A + R_B + R_C = 24.69\ \Omega$.

$$R_1 = \frac{R_A \cdot R_B}{R} = 1.51\ \Omega$$

$$R_2 = \frac{R_B \cdot R_C}{R} = 0.891\ \Omega$$

$$R_3 = \frac{R_C \cdot R_A}{R} = 0.0684\ \Omega$$

$$\text{Then, } R_{Th} = (12 + R_1) \parallel (10 + R_2) + R_3 = 6.098\ \Omega.$$

Define three nodal voltages on the original circuit after naming the bottom node as the reference node: V_1 , V_2 , V_{oc} . Then,

$$0 = \frac{V_1 - 9}{11} + \frac{V_1}{2} + \frac{V_1 - V_{oc}}{12} + \frac{V_1 - V_2}{22}$$

$$0 = \frac{V_2}{1} + \frac{V_2 - V_1}{22} + \frac{V_2 - V_{oc}}{10}$$


$$0 = \frac{V_{oc} - V_2}{10} + \frac{V_{oc} - V_1}{12}$$

$$\text{Solving, } V_{oc} = -606.7\ \text{mV}$$

$$(b) P_{1\Omega} = [0.6067/7.098]^2 (1) = 7.306\ \text{mW}$$

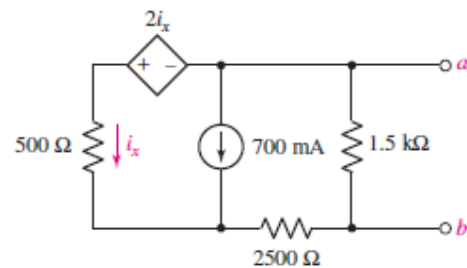Problem 5 (10 points)

Determine the Norton equivalent of the circuit drawn in Fig. 5.81 as seen by terminals a and b . (There should be no dependent sources in your answer.)



■ FIGURE 5.81

We short the terminals of the network and compute the short circuit current. To do this, define two clockwise mesh currents (the 1500 Ω resistor is shorted out).

$$500i_1 + 2i_x + 2500i_2 = 0 \quad [1]$$

$$i_1 - i_2 = 0.7 \quad [2]$$

$$i_1 = -i_x \quad [3]$$

Or equivalently:

$$-500i_x + 2i_x + 2500i_2 = 0 \quad [1]$$

$$-i_x - i_2 = 0.7 \quad [2]$$

Solving, $i_2 = i_{sc} = i_N = -116.3 \text{ mA}$

Next, we zero out the independent source and connect a 1 A test source across the terminals a and b such that 1 A flows into a . Define v_{test} with the '+' reference at terminal a , and the cathode at terminal b . Then,

$$-2i_x + 500i_x + 2500i_x + 1500(i_x - 1) = 0$$

so

$$i_x = 0.333 \text{ A}$$

Solving, $v_{test} = 1500(1 - i_x) = 1000 \text{ V}$ so

$$R_{TH} = v_{test}/1 \text{ A} = 1000 \Omega$$