

Solution Training Second Partial Integrator Exam

TE1002 Circuits 1

Dr. Juan Manuel CAMPOS

Tecnológico de Monterrey

Name _____

Problem 1

For the circuit of Fig. 4.73, determine the mesh current i_1 and the power dissipated by the $1\ \Omega$ resistor.

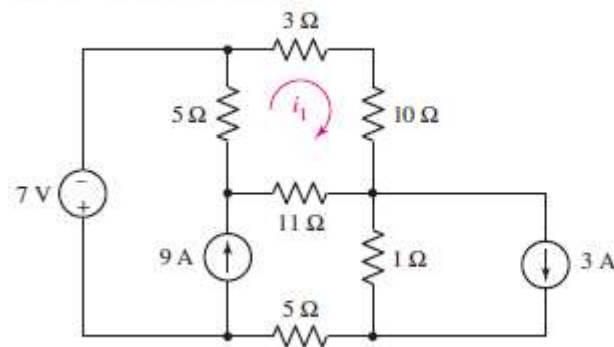


FIGURE 4.73

Solution Problem 1

Define (left to right) three clockwise mesh currents i_2 , i_3 and i_4 . Then, we may create a supermesh from meshes 2 and 3. By inspection, $i_4 = 3\text{ A}$.

Our mesh/supermesh equations are:

$$7 + 5i_2 - 5i_1 + 11i_3 - 11i_1 + (1)i_3 - (1)i_4 + 5i_3 = 0$$

$$-5i_2 + (3 + 5 + 10 + 11)i_1 - 11i_3 = 0$$

$$i_3 - i_2 = 9$$

Solving,

$$i_1 = -874.3\text{ mA}$$

$$i_2 = -7.772\text{ A}$$

$$i_3 = 1.228\text{ A}$$

$$i_4 = 3\text{ A}$$

Thus, the $1\ \Omega$ resistor dissipates $P_{1\Omega} = (1)(i_4 - i_3)^2 = 3.141\text{ W}$

Problem 2

- (a) Employ superposition to determine the individual contribution from each independent source to the current i_x as labeled in the circuit shown in Fig. 5.57.
 (b) Compute the power absorbed by each $1\ \Omega$ resistor.

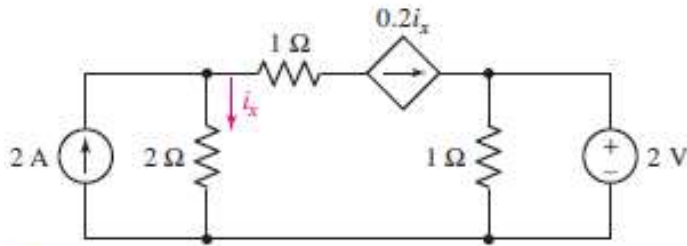


FIGURE 5.57

Solution Problem 2

- (a) Begin by short-circuiting the voltage source.

$$\text{KCL yields } 2 = i'_x + 0.2i'_x \quad \text{or } i'_x = \frac{2}{1.2} = 1.667 \text{ A}$$

Now, open-circuit the independent current source instead.

$$i''_x = -0.2i''_x \quad \text{therefore } i''_x = 0$$

$$\text{Hence, } i_x = i'_x + i''_x = 1.667 \text{ A}$$

- (b) $P_{1\Omega(\text{left})} = (1)(0.2i_x)^2 = 111 \text{ mW}$

$$P_{1\Omega(\text{right})} = \frac{(2)^2}{1} = 4 \text{ W}$$

Problem 3

(a) Using repeated source transformations, reduce the circuit of Fig. 5.62 to a voltage source in series with a resistor, both of which are in series with the $6\text{ M}\Omega$ resistor. (b) Calculate the power dissipated by the $6\text{ M}\Omega$ resistor using your simplified circuit.

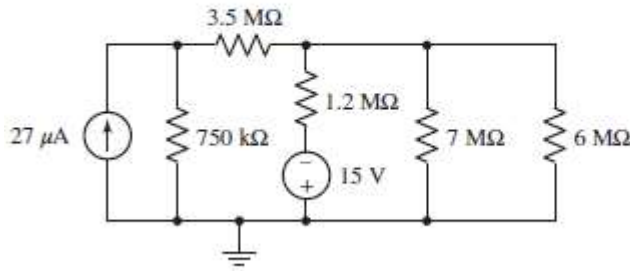


FIGURE 5.62

Solution Problem 3

(a) Perform the following steps in order:


Combine the $27\text{ }\mu\text{A}$ and $750\text{ k}\Omega$ to obtain 20.25 V in series with $750\text{ k}\Omega$ in series with $3.5\text{ M}\Omega$.

Convert this series combination to a $4.25\text{ M}\Omega$ resistor in parallel with a $4.765\text{ }\mu\text{A}$ source, arrow up.

Convert the $15\text{ V}/1.2\text{ M}\Omega$ series combination into a $12.5\text{ }\mu\text{A}$ source (arrow down) in parallel with $1.2\text{ M}\Omega$. This appears in parallel with the current source from above as well as the $7\text{ M}\Omega$ and $6\text{ M}\Omega$.

Combine: $4.25\text{ M}\Omega \parallel 1.2\text{ M}\Omega \parallel 7\text{ M}\Omega = 0.8254\text{ M}\Omega$. This, along with the $-12.5\text{ }\mu\text{A} + 4.765\text{ }\mu\text{A}$ yield a $-7.735\text{ }\mu\text{A}$ source (arrow up) in parallel with $825.4\text{ k}\Omega$ in parallel with $6\text{ M}\Omega$.

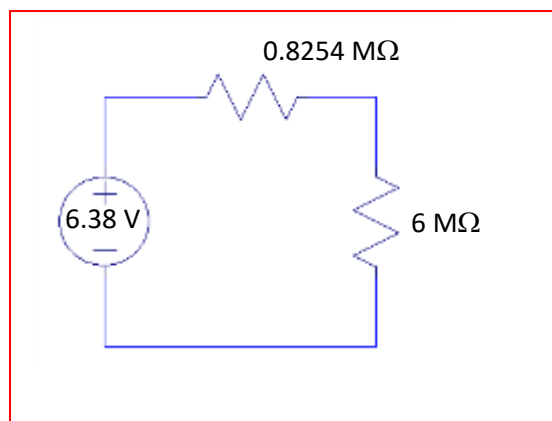Convert the current source and $825.4\text{ k}\Omega$ resistor into a 6.38 V source ('+' reference up) in series with $825.4\text{ k}\Omega$ and $6\text{ M}\Omega$.



$$(b) P_{6\text{ M}\Omega} = \left[\frac{6.38}{6 \times 10^6 + 825.4 \times 10^3} \right]^2 (6 \times 10^6) = \boxed{5.24\text{ }\mu\text{W}}$$

Problem 4

Determine the Thévenin equivalent of the network shown in Fig. 5.74 as seen looking into the two open terminals.

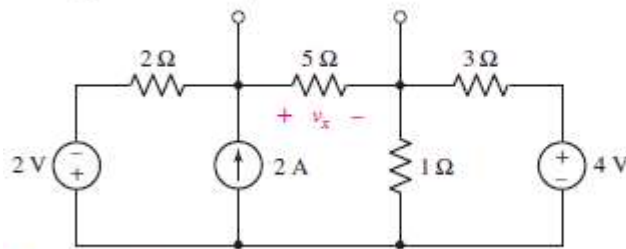


FIGURE 5.74

Solution Problem 4

Define three clockwise mesh currents i_1 , i_2 , i_3 starting on the left.

Then

$$2 + 2i_1 + 6i_2 - i_3 = 0 \quad [1]$$

$$-i_2 + 4i_3 + 4 = 0 \quad [2]$$

$$i_2 - i_1 = 2 \quad [3]$$

Solving,

$$i_2 = 129 \text{ mA. Hence, } v_{oc} = v_x = 5i_2 = 645.2 \text{ mV}$$

Next, short the voltage sources and open circuit the current source. Then,

$$R_{th} = 5 \parallel (2 + 3 \parallel 1) = 1.774 \Omega$$

Problem 5

Determine the Thévenin and Norton equivalents of the circuit shown in Fig. 5.83, as seen by an unspecified element connected between terminals a and b .

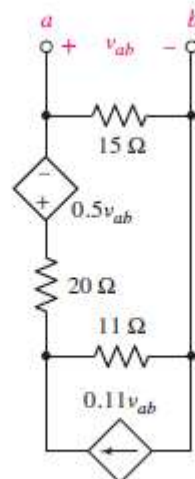


FIGURE 5.83

Solution Problem 5

Rotate the diagram 90° clockwise. Connect a 1 A source between a and b such that the head of the arrow points to terminal a . Define a clockwise mesh current i_2 flowing into the '+' reference of the dependent voltage source. Then,

$$11(i_2 - 0.11v_{ab}) + 20i_2 + 0.5v_{ab} + 15(i_2 + 1) = 0$$

where

$$v_{ab} = 15(i_2 + 1)$$

Solving, $v_{ab} = 13.15 \text{ V}$.

Hence, $R_{Th} = v_{ab}/1 = 13.15 \Omega$.

Since there is no independent source in the network, this represents both the Thévenin and Norton equivalent.

Problem 6

(a) Determine the two-component Thévenin equivalent of the network in Fig. 5.102. (b) Calculate the power dissipated by a 1Ω resistor connected between the open terminals.

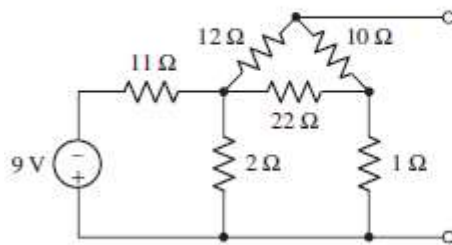


FIGURE 5.102

Solution Problem 6

(a) Shorting the 9 V source leaves the 11Ω in parallel with 2Ω . Name this $R_A = 1.69 \Omega$.

Then, $R_B = 22 \Omega$, and $R_C = 1 \Omega$.

Converting this to a T network, with $R = R_A + R_B + R_C = 24.69 \Omega$.

$$R_1 = \frac{R_A \cdot R_B}{R} = 1.51 \Omega$$

$$R_2 = \frac{R_B \cdot R_C}{R} = 0.891 \Omega$$

$$R_3 = \frac{R_C \cdot R_A}{R} = 0.0684 \Omega$$

Then, $R_{Th} = (12 + R_1) \parallel (10 + R_2) + R_3 = 6.098 \Omega$.

Define three nodal voltages on the original circuit after naming the bottom node as the reference node: V_1 , V_2 , V_{oc} .

Then,

$$0 = \frac{V1-9}{11} + \frac{V1}{2} + \frac{V1-Voc}{12} + \frac{V1-V2}{22}$$

$$0 = \frac{V2}{1} + \frac{V2-V1}{22} + \frac{V2-Voc}{10}$$

$$0 = \frac{Voc-V2}{10} + \frac{Voc-V1}{12}$$

Solving, $V_{oc} = -606.7 \text{ mV}$

(b) $P_{1\Omega} = [0.6067/7.098]^2 (1) = 7.306 \text{ mW}$