

Quiz 8

Electrical Circuits 1


TE1002

Tecnológico de Monterrey

Dr. Juan-Manuel CAMPOS-SANDOVAL

Name _____

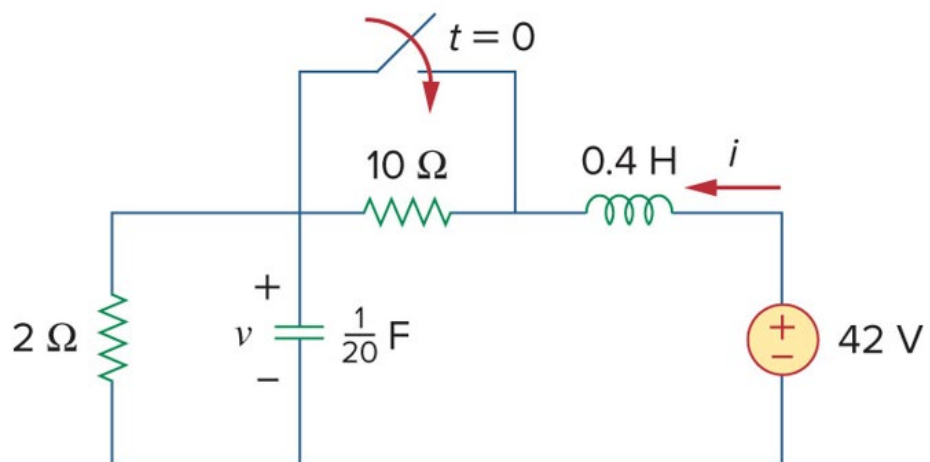Find $i(0^+)$, $v(0^+)$, $di(0^+)/dt$ and $dv(0^+)/dt$.



Answer: (a) 3.5 A, 7 V, (b) 87.5 A/s, 0 V/s, (c) 21 A, 42 V.